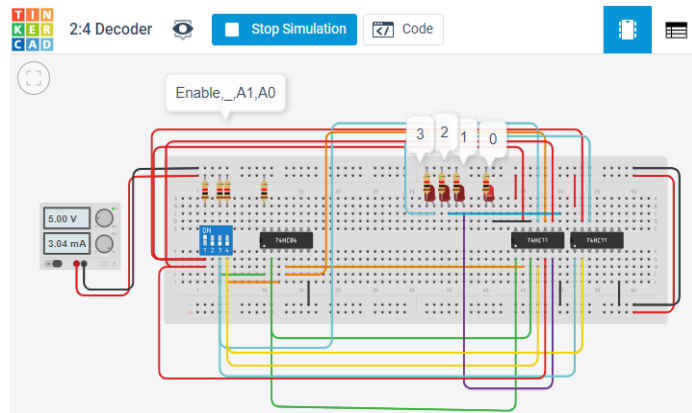


Mayukh Barman Ray, CSE, Roll: 04 , 2<sup>nd</sup> year

## 2:4 Decoder




design by:  
**mayukh barman ray**

Edited 11/7/20, Created 11/4/20

Tinker this

2:4 Decoder


Like 1

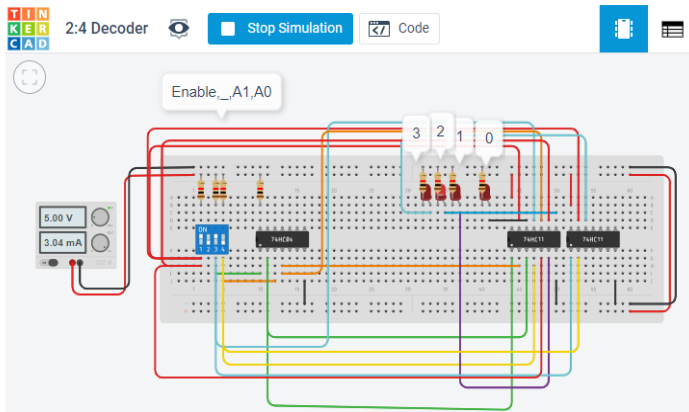

design by:  
**mayukh barman ray**

Edited 11/7/20, Created 11/4/20

Tinker this

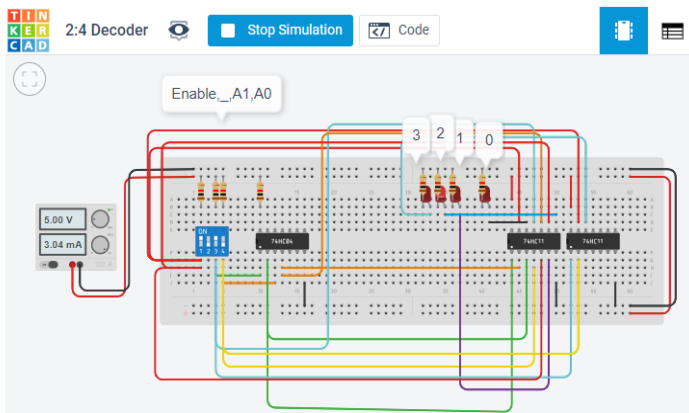


design by:  
**mayukh barman ray**

Edited 11/7/20, Created 11/4/20

Tinker this

Mayukh Barman Ray, CSE, Roll: 04 , 2<sup>nd</sup> year


## 4:1 Multiplexer

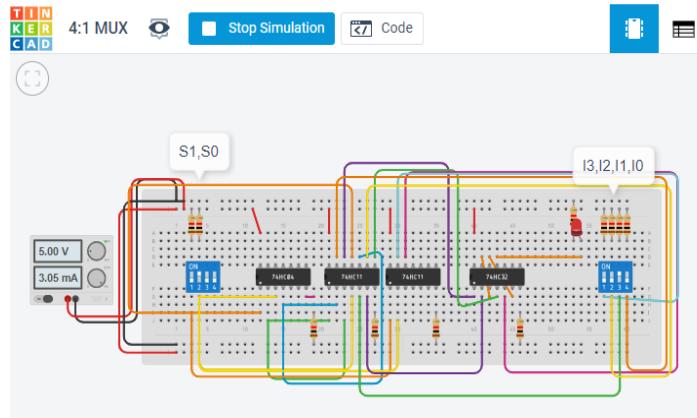

design by:  
**mayukh barman ray**

Edited 11/17/20, Created 11/17/20


[Tinker this](#)

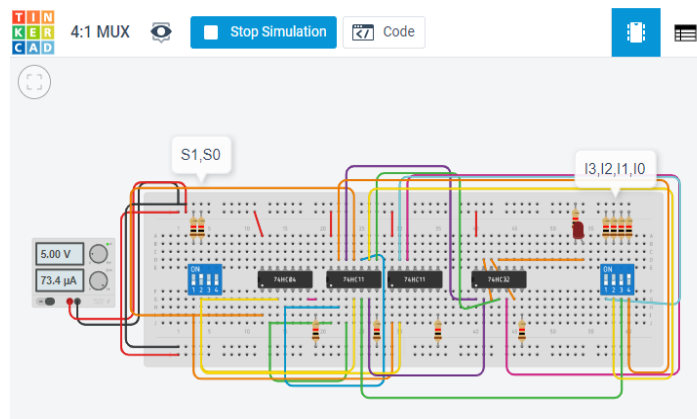

design by:  
**mayukh barman ray**

Edited 11/17/20, Created 11/17/20

[Tinker this](#)

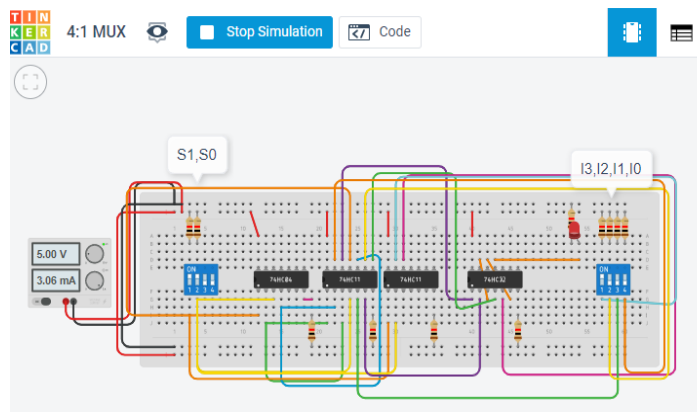

design by:  
**mayukh barman ray**

Edited 11/17/20, Created 11/17/20

[Tinker this](#)

## QUESTIONNAIRES:-

① Design Full Adder using 3 to 8 decoder.

Truth table of Full Adder:


INPUT			OUTPUT		
A	B	C	SUM	CARRY	
0	0	0	0	0	$m_0$
0	0	1	1	0	$m_1$
0	1	0	1	0	$m_2$
0	1	1	0	1	$m_3$
1	0	0	1	0	$m_4$
1	0	1	0	1	$m_5$
1	1	0	0	1	$m_6$
1	1	1	1	1	$m_7$

The boolean function for the adder sum,

$$F(A, B, C) = \sum m(1, 2, 4, 7)$$

The boolean function for the adder carry,

$$F(A, B, C) = \sum m(3, 5, 6, 7)$$

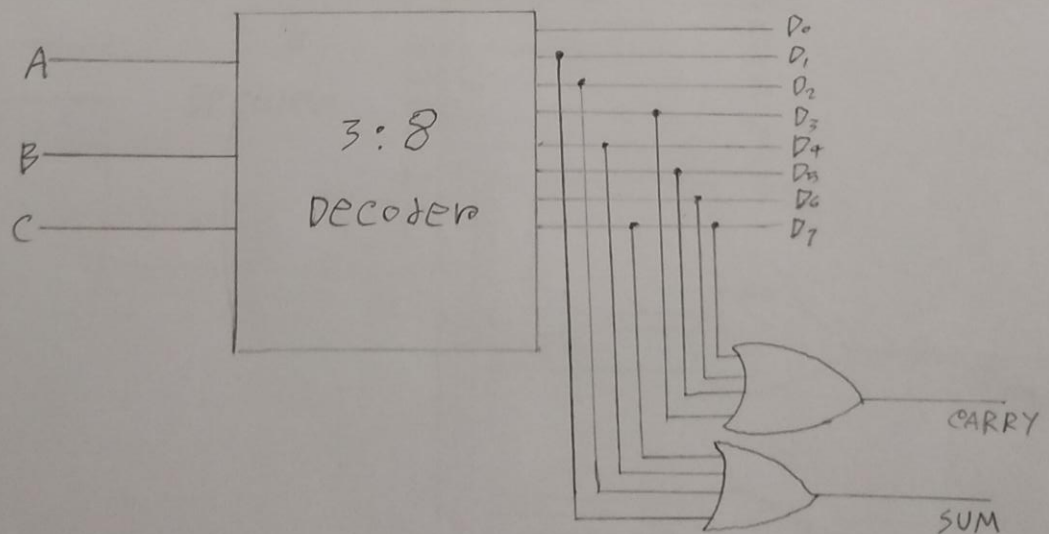

② Design Full Subtractor using 3 to 8 decoder.


Ans: Truth Table of Full Subtractor:

INPUT			OUTPUT		
A	B	C	D	Bout	
0	0	0	0	0	$m_0$
0	0	1	1	1	$m_1$
0	1	0	1	1	$m_2$
0	1	1	0	1	$m_3$
1	0	0	1	0	$m_4$
1	0	1	0	0	$m_5$
1	1	0	0	0	$m_6$
1	1	1	1	1	$m_7$

The boolean function for the subtractor difference  
 $F(A, B, C) = \sum m(1, 2, 4, 7)$

The boolean function for the Borrow out in subtractor is,

$$F(A, B, C) = \sum m(1, 2, 3, 7)$$

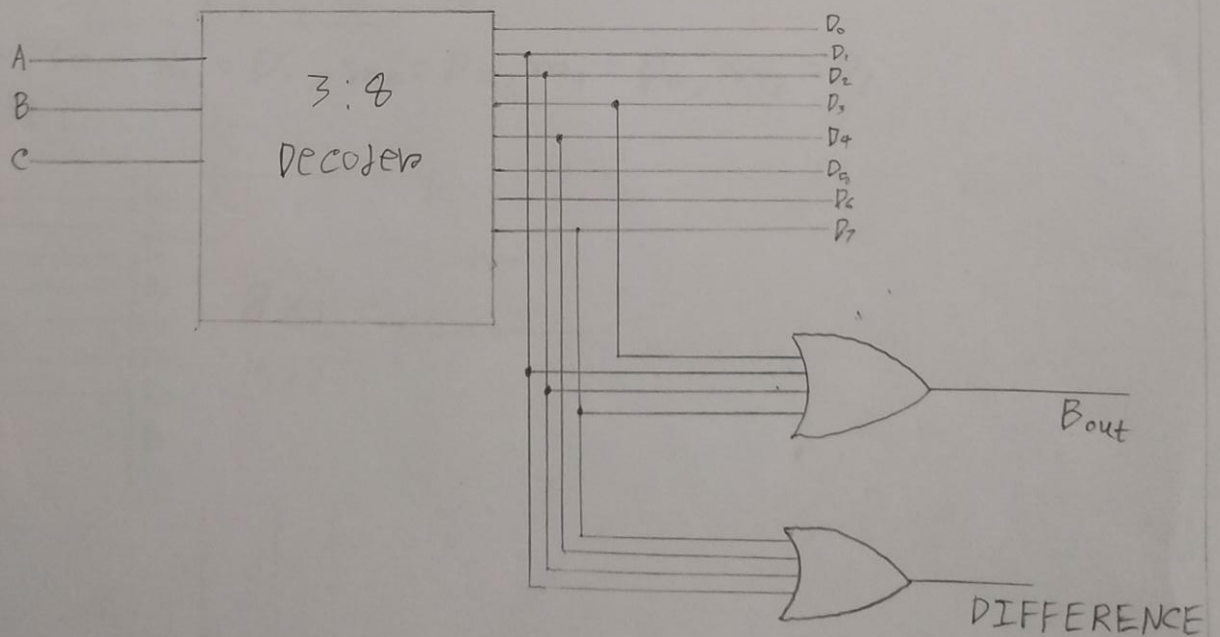



③ Design and implement  $F(A, B, C) = \sum m(1, 2, 4, 7)$  using suitable MUX.

Ans: In a multiplexer  $8 \times 1$ , there are 3 select line, 8 inputs and 1 output.


Let the select lines be  $C, B, A$ . Input lines be  $D_0, D_1, D_2, \dots, D_7$  and output be  $F$ .

Truth Table:

INPUT			F	
C	B	A		
0	0	0	$D_0$	$m_0$
0	0	1	$D_1$	$m_1$
0	1	0	$D_2$	$m_2$
0	1	1	$D_3$	$m_3$
1	0	0	$D_4$	$m_4$
1	0	1	$D_5$	$m_5$
1	1	0	$D_6$	$m_6$
1	1	1	$D_7$	$m_7$

We see  $m_1 = D_1, m_2 = D_2, m_4 = D_4, m_7 = D_7$

circuit:

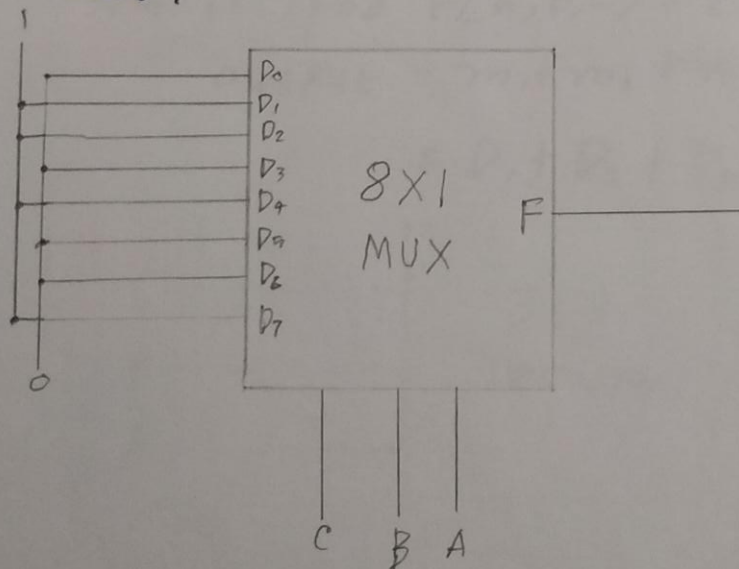

④ Design and implement  $F(A,B,C) = \sum m(1,2,4,7)$  using suitable decoder.

Ans: In a 3:8 active high decoder there are 3 input lines and 8 output lines.

Let, the input lines be C, B, A

Let, the output lines be  $D_0, D_1, D_2, \dots, D_7$

Let, the output out of  $D_0, D_1, D_2, \dots, D_7$  with high voltage be F.

INPUT			OUTPUT								F	
C	B	A	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$		
0	0	0	1	0	0	0	0	0	0	0	$D_0$	$m_0$
0	0	1	0	1	0	0	0	0	0	0	$D_1$	$m_1$
0	1	0	0	0	1	0	0	0	0	0	$D_2$	$m_2$
0	1	1	0	0	0	1	0	0	0	0	$D_3$	$m_3$
1	0	0	0	0	0	0	1	0	0	0	$D_4$	$m_4$
1	0	1	0	0	0	0	0	1	0	0	$D_5$	$m_5$
1	1	0	0	0	0	0	0	0	1	0	$D_6$	$m_6$
1	1	1	0	0	0	0	0	0	0	1	$D_7$	$m_7$

Simplifying  $F(A,B,C) = \sum m(1,2,4,7)$

output =  $m_1 + m_2 + m_4 + m_7$  (each minterm been 1)

$$= D_1 + D_2 + D_4 + D_7$$

